



EAST WEST UNIVERSITY

## Project – 1

Project Title: 2's complementor

Course: CSE345

Title: Digital Logic Design

Section: 02

Semester: Summer 2020

Submitted To:

Musharrat Khan

Senior Lecturer

Department of

Computer Science and Engineering

Submitted by:

Md. Moniruzzaman Shanto

ID: 2018-1-60-075

Department of

Computer Science and Engineering

Date of Submission: 24/09/2020.

- ❖ **Problem Statement:** Objective of project 1 is to create a 2's Complementor which will take 4-bit binary number as input and in output section it will generate 4 bit 2's complement of given input.
- ❖ **Design details:** Truth table has been constructed according to the 2's complement of each binary number. After that Expressions of each output has been constructed using K-map method. Using these expressions of output P, Q, R, S diagram of the circuit has been constructed.

✓ **Truth Table:**

Value	Binary				2's Complement			
	A	B	C	D	P	Q	R	S
0	0	0	0	0	0	0	0	0
1	0	0	0	1	1	1	1	1
2	0	0	1	0	1	1	1	0
3	0	0	1	1	1	1	0	1
4	0	1	0	0	1	1	0	0
5	0	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	0
7	0	1	1	1	1	0	0	1
8	1	0	0	0	1	0	0	0
9	1	0	0	1	0	1	1	1
10	1	0	1	0	0	1	1	0
11	1	0	1	1	0	1	0	1
12	1	1	0	0	0	1	0	0
13	1	1	0	1	0	0	1	1
14	1	1	1	0	0	0	1	0
15	1	1	1	1	0	0	0	1

Table 1: Truth Table for 2's Complementor.

✓ **K-map for output P:**

	C D			
A B	0 0	0 1	1 1	1 0
0 0	0	1	1	1
0 1	1	1	1	1
1 1	0	0	0	0
1 0	1	0	0	0

Table 2: Representation of truth table on k-map for output P.

$$\begin{aligned}
 \text{Expression of } P &= A'D + A'C + A'B + AB'C'D' \\
 &= A'(B+C+D) + A(B+C+D)' \\
 &= A \oplus (B+C+D)
 \end{aligned}$$

✓ **K-map for output Q:**

	C D			
A B	0 0	0 1	1 1	1 0
0 0	0	1	1	1
0 1	1	0	0	0
1 1	1	0	0	0
1 0	0	1	1	1

Table 3: Representation of truth table on k-map for output Q.

$$\begin{aligned}
 \text{Expression of } Q &= BC'D' + B'D + B'C \\
 &= B(C+D)' + B'(C+D) \\
 &= B \oplus (C+D)
 \end{aligned}$$

✓ **K-map for output R:**

	C D			
A B	0 0	0 1	1 1	1 0
0 0	0	1	0	1
0 1	0	1	0	1
1 1	0	1	0	1
1 0	0	1	0	1

Table 4: Representation of truth table on k-map for output R.

Expression of  $R = C'D + CD'$

$$= C \oplus D$$

✓ **K-map for output S:**

	C D			
A B	0 0	0 1	1 1	1 0
0 0	0	1	1	0
0 1	0	1	1	0
1 1	0	1	1	0
1 0	0	1	1	0

Table 5: Representation of truth table on k-map for output S.

Expression of  $S = D$

### ❖ Circuit Diagram:

 


Figure 1: Schematic circuit.

### ❖ Behavioral Verilog Code:

```
1 module code(input A,B,C,D,output P,Q,R,S);
2   assign P=A ^ (B | C | D);
3   assign Q=B ^ (C | D);
4   assign R=C ^ D;
5   assign S=D;
6   endmodule
```

Figure 2: Behavioral Verilog code using Continuous assign statement.

```

1  module code(input A,B,C,D, output reg P,Q,R,S);
2  always@ (A,B,C,D) begin
3      P=0;
4      Q=0;
5      R=0;
6      S=D;
7      if(A ^ (B | C | D)) P = 1;
8      if(B ^ (C | D)) Q = 1;
9      if(C^D) R = 1;
10 end
11 endmodule
12

```

Figure 3: Behavioral Verilog code using procedural model.

### ❖ Simulation Result:

 


Figure 4: Simulation output.